



**Faculty Of Engineering and Technology**  
**Electrical And Computer Engineering Department**  
**ADVANCED DIGITAL DESIGN (ENCS3310)**

---

**COURSE PROJECT**  
**Report**  
**4-bit Arithmetic Unit**

---

**Prepared by:** Nicola Abu Shaibeh 1190843

**Instructor:** Dr. Abdellatif Abu-Issa

**Date:** 22 / 8 / 2022

# 1. BRIEF INTRODUCTION AND BACKGROUND

In this project, we learn about the concept and design of a 4-bit Arithmetic Unit, that contains 4 4x1 multiplexers and 4 full adders that will be joined to gather to build it, in addition to implanting it utilizing basic logic gates with specific delays, as well as writing structural Verilog code to describe the full circuit and for functional verification with the purpose of testing out the results of all possible values entering the Arithmetic Unit. This Arithmetic circuit performs seven different arithmetic microoperations using 3 selectors ( $S_0, S_1, C_{in}$ ) to choose the operation as shown in the table below. We utilize 4 multiplexers and 4-bit ripple carry adder to build this circuit

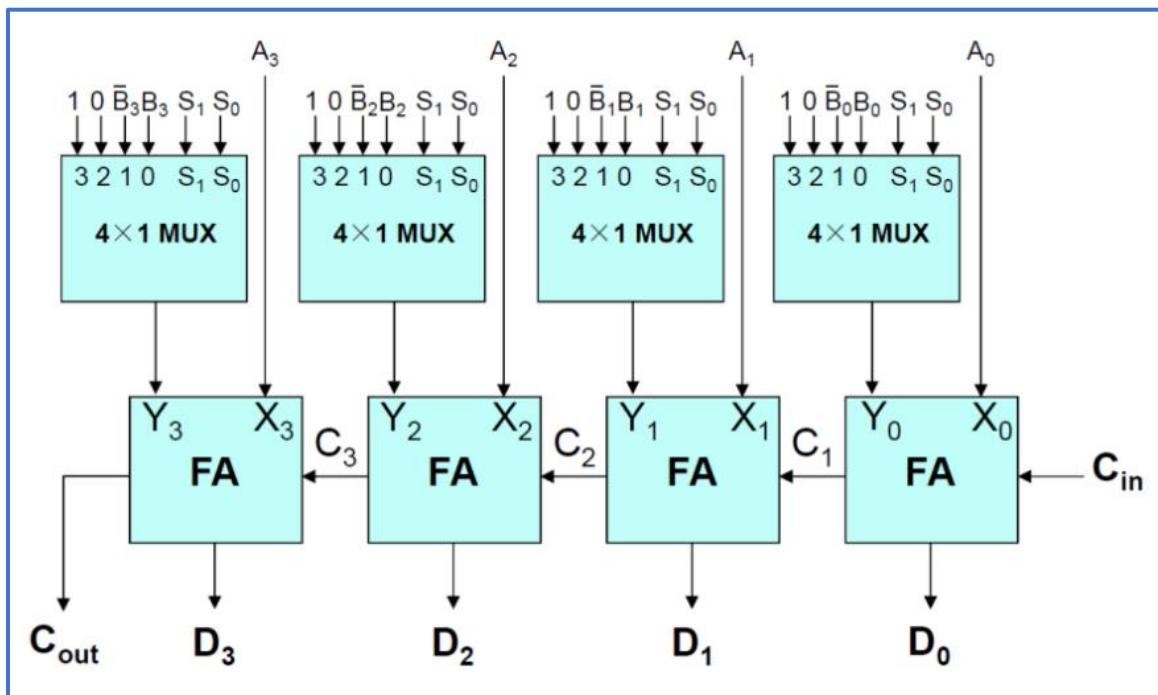


FIGURE 1: 4-BIT ARITHMETIC UNIT

# CONTENTS

|  |    |
|--|----|
| 1. Brief introduction and background ..... | 1  |
| 2. Design philosophy .....                 | 4  |
| • Gates.....                               | 4  |
| • Multiplexer .....                        | 4  |
| 2.1 Stage 1 .....                          | 5  |
| 2.2 Stage 2 .....                          | 6  |
| 2.3 Registers .....                        | 7  |
| 2.4 Built-in Self-Test .....               | 8  |
| • Test analyzer.....                       | 8  |
| • Test generator .....                     | 9  |
| 3. Results .....                           | 10 |
| 3.1. STAGE 1 .....                         | 10 |
| Rising an error .....                      | 11 |
| 3.2. STAGE 2 .....                         | 11 |
| Rising an error .....                      | 12 |
| 4. Conclusion and Future works .....       | 13 |
| APPENDIX .....                             | 14 |

## LIST OF FIGURES

|  |    |
|--|----|
| FIGURE 1: 4-BIT ARITHMETIC UNIT.....               | 1  |
| FIGURE 2: RIPPLE CARRY ADDERS.....                 | 5  |
| FIGURE 3: 1-BIT FULL ADDER CIRCUIT .....           | 5  |
| FIGURE 4: RIPPLE CARRY ADDER .....                 | 6  |
| FIGURE 5: PARTIAL FULL ADDER.....                  | 6  |
| FIGURE 6: LOOK AHEAD CODE.....                     | 7  |
| FIGURE 7: REGISTER.....                            | 8  |
| FIGURE 8: TEST ANALYZER CODE.....                  | 8  |
| FIGURE 9: TEST GENERATOR .....                     | 9  |
| FIGURE 10: RESULT STAGE 1 WAVE FORM.....           | 10 |
| FIGURE 11: RESULT STAGE 1 SELF-TEST ALU CODE ..... | 10 |
| FIGURE 12: RESULT STAGE 1 ERROR WAVE.....          | 11 |
| FIGURE 13: RESULT STAGE 1 ERROR OCCURED .....      | 11 |
| FIGURE 14: RESULT STAGE 2 WAVE FORM.....           | 11 |
| FIGURE 15: RESULT STAGE 2 SELF-TEST ALU CODE ..... | 12 |
| FIGURE 16: RESULT STAGE 2 ERROR WAVE.....          | 12 |
| FIGURE 17: RESULT STAGE 2 ERROR OCCURED .....      | 12 |

## 2. DESIGN PHILOSOPHY

- GATES

A logic gate is an idealized model of computation or physical electronic device implementing a Boolean function, a logical operation performed on one or more binary inputs that produce a single binary output. Depending on the context, the term may refer to an ideal logic gate, one that has for instance zero rise time and unlimited fan-out, or it may refer to a non-ideal physical device.

The library element multiplexers and full adders was built with those gates, at given delays.

| Gate     | Delay |
|----------|-------|
| Inverter | 3 ns  |
| NAND     | 5 ns  |
| NOR      | 5 ns  |
| AND      | 7 ns  |
| OR       | 7 ns  |
| XNOR     | 9 ns  |
| XOR      | 11 ns |

- MULTIPLEXER

Multiplexing is the process of combining one or more signals and transmitting on a single channel. A digital switch also known as a data selector, the multiplexer or MUX is a switch. With several input lines, one output line, the output of the mux will be input b for the full adder

- In this project, the 4-bit Arithmetic Unit implementation in two stages of complexity, first by using ripple carry adder and second by using carry look ahead on 4-bit groups.

## 2.1 STAGE 1

In this stage we will use ripple carry adder, that was constructed from 1-bit full adder which was built from basic gates given. Then we will complete functional verification to demonstrate the ALU.

 


FIGURE 3: 1-BIT FULL ADDER CIRCUIT

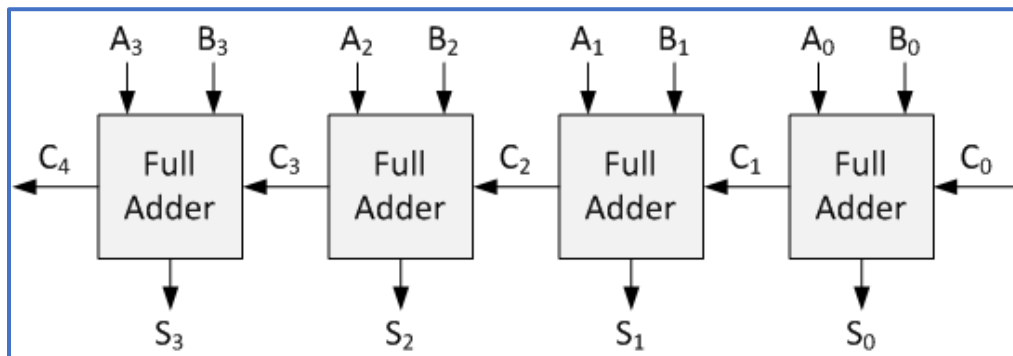


FIGURE 2: RIPPLE CARRY ADDERS

After that we will calculate the maximum latency after the simulation of the circuit to determine the maximum frequency of normal mode clock that can be applied to the flipflop in the circuit, subsequently we should make an error in the circuit and then do a verification that will find the error and make a task that print to console when logical error occur and causes an unexpected output.

```

module full_adder(a,b,cin,s,cout); |
    input a,b,cin;
    output cout,s;
    wire [2:0]w;

    xor #(12ns) x1(w[0],a,b);
    xor #(12ns) x2(s,w[0],cin);
    and #(8ns) a1(w[1],w[0],cin);
    and #(8ns) a2(w[2],a,b);
    or #(8ns) o1(cout,w[1],w[2]);
endmodule

module ripple_carry_adder(a,b,s,cin,cout);
    input [3:0]a;
    input [3:0]b;
    input cin;
    output [3:0]s;
    output cout;
    wire [3:0]C;

    full_adder f1(a[0],b[0],cin,s[0],C[0]);
    full_adder f2(a[1],b[1],C[0],s[1],C[1]);
    full_adder f3(a[2],b[2],C[1],s[2],C[2]);
    full_adder f4(a[3],b[3],C[2],s[3],cout);
endmodule

```

FIGURE 4: RIPPLE CARRY ADDER

## 2.2 STAGE 2

In this stage we will use carry look ahead, that accelerates addition on 4-bit groups. Then we will complete functional verification to demonstrate the ALU.

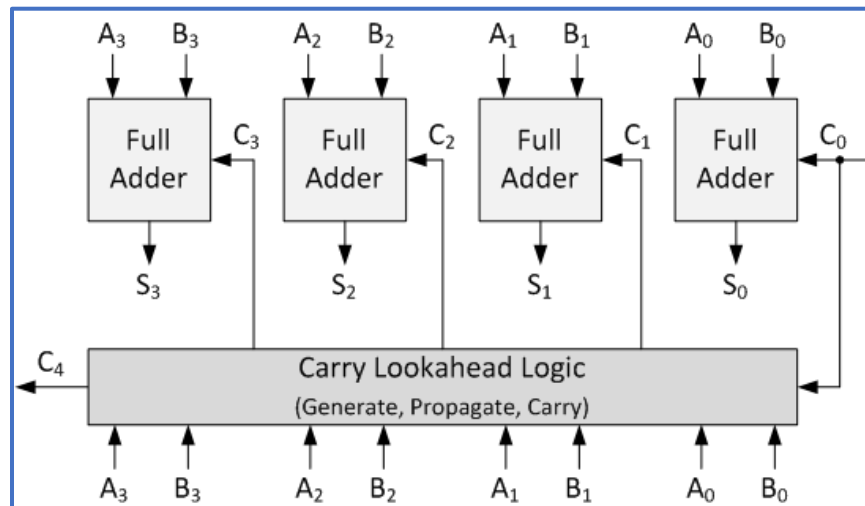


FIGURE 5: PARTIAL FULL ADDER

In normal ripple adders, the carry of the output of each full adder is given as a carry input to the next higher-order state. Henceforth, these adders it is not possible to produce carry and sum outputs of any state without a carry input is available for that state. Subsequently we will calculate the maximum latency after the simulation of the circuit to determine the maximum frequency of normal mode clock that can be applied to the flipflop in the circuit, subsequently we should make an error in the circuit and then do a verification that will find the error and make a task that print to console when logical error occur and causes an unexpected output.

```
module LookAhead(A,B,c_0,S,c_4);
  input [3:0]A,B;
  input c_0;
  output [3:0]S;
  output c_4;
  wire [3:0]P,G;
  wire [3:1]C;
  wire [3:0]w;
  wire [3:0]ig;
  xor #(11ns) x1(P[0],A[0],B[0]);
  xor #(11ns) x2(P[1],A[1],B[1]);
  xor #(11ns) x3(P[2],A[2],B[2]);
  xor #(11ns) x4(P[3],A[3],B[3]);
  and #(7ns) a1(G[0],A[0],B[0]);
  and #(7ns) a2(G[1],A[1],B[1]);
  and #(7ns) a3(G[2],A[2],B[2]);
  and #(7ns) a4(G[3],A[3],B[3]);
  full_adder f1(A[0],B[0],c_0,S[0],ig[0]);
  full_adder f2(A[1],B[1],C[1],S[1],ig[1]);
  full_adder f3(A[2],B[2],C[2],S[2],ig[2]);
  full_adder f4(A[3],B[3],C[3],S[3],ig[3]);
  and #(7ns) a5(w[0],P[0],c_0);
  or #(7ns) o1(C[1],G[0],w[0]);
  and #(7ns) a7(w[1],P[1],C[1]);
  and #(7ns) a8(w[2],P[2],C[2]);
  and #(7ns) a9(w[3],P[3],C[3]);
  or #(7ns) o2(C[2],G[1],w[1]);
  or #(7ns) o3(C[3],G[2],w[2]);
  or #(7ns) o4(c_4,G[3],w[3]);
endmodule
```

FIGURE 6: LOOK AHEAD CODE

## 2.3 REGISTERS

We build the registers utilizing d-flipflop to synchronize the input of the ALU, as well as synchronizing the output.



```

module DFF (Q,D,CLK);
    output Q;
    input D,CLK;
    reg Q;
    always @(posedge CLK)
        Q = D;
endmodule

module registerIN(Q,D,CLK);
    parameter n = 15;
    input [n-1:0]D;
    input CLK;
    output [n-1:0]Q;

    genvar i;

    generate
    for (i=0;i<=n-1;i=i+1)
        begin:addbit
            DFF stage(Q[i],D[i],CLK);
        end
    endgenerate
endmodule

```

FIGURE 7: REGISTER

## 2.4 BUILT-IN SELF-TEST

Until now we have assumed that testing of the logic circuits in each stage is done by externally applying the test inputs and comparing the results with the expected behavior of the circuit. This requires connecting external equipment to the circuit under test.

### • TEST ANALYZER

Test analyzer ensures the output of the test generator same as the output of the circuit and raise an error if the output is not the same.

```

module TestAnalyzer(CLK,genin,circin);
    input CLK;
    input [3:0]genin;
    input [3:0]circin;

    reg [8:0]check;

    always @(posedge CLK)
        begin
            if (check != circin)
                begin
                    $display("Error Occured at TIME = %t", $time);
                    // $finish;
                end
            check = genin;
        end
endmodule

```

FIGURE 8: TEST ANALYZER CODE

- TEST GENERATOR

This generator builds on behavioral logic of the ALU micro-operations, to test the all operation on A and B, also it sends output to test analyzer and to the main circuit to compare them.

```
module TestGenerator(a, b, d, s0, s1, cin, cout, CLK);
    input CLK;
    output reg [3:0] a, b;
    output reg s0, s1, cin;
    output reg [3:0] d;
    output cout;
    assign bnot = ~b;
    always @(posedge CLK)

        begin
            case({s0,s1,cin})
            3'b000: d = a + b;
            3'b001: d = a + b + 1'b1;
            3'b010: d = a + bnot;
            3'b011: d = a + bnot + 1'b1;
            3'b100: d = a;
            3'b101: d = a + 1'b1;
            3'b110: d = a - 1'b1;
            3'b111: d = a;
            endcase

            {s0, s1, cin} = {s0, s1, cin} + 3'b001;

        end

    initial
        begin
            a = 4'b0100;
            b = 4'b0010;
            {s0, s1, cin} = 3'b000;
        end
endmodule
```

FIGURE 9: TEST GENERATOR

### 3.RESULTS

- In this section, simulation output of the Arithmetic Unit and the maximum delay are provided.

#### 3.1. STAGE 1

After testing the ALU utilizing the ripple adder, I calculate the maximum latency possible time to prevent the delay problems, its (114) nanoseconds, thus the maximum frequency of normal-mode clock is 8.77MHz.

Also, as we can see from figure below, I made A and B as a constant A=4 and B=2, and changing the selectors (s0, s1, cin) to test all the microoperations on the ALU. As we can see all the result are correct and stable as needed.

 


FIGURE 10: RESULT STAGE 1 WAVE FORM

```

module SelfTestALU();
    reg CLK;
    reg [3:0] a,b;
    reg s0,s1,cin;
    wire [3:0]circuit_out,generator_out;
    reg cout, Cout;

    generator g(a, b, generator_out, s0, s1, cin, cout, CLK);

    ALU al(a, b, circuit_out, s0, s1, cin, Cout, CLK);

    analyzer z(CLK,generator_out,circuit_out);

    initial
        begin
            CLK = 0;
            repeat(200)
                #100ns CLK = ~CLK;
        end
endmodule

```

FIGURE 11: RESULT STAGE 1 SELF-TEST ALU CODE



```

module SelfTestALU_LA();
    reg CLK;
    reg [3:0] a,b;
    reg s0,s1,cin;
    wire [3:0]circuit_out,generator_out;
    reg cout, Cout;

    generator g(a, b, generator_out, s0, s1, cin, cout, CLK);

    ALU_LA la(a, b, circuit_out, s0, s1, cin, Cout, CLK);

    analyzer z(CLK,generator_out,circuit_out);

    initial
        begin

            CLK = 0;
            repeat(200)
                #100ns CLK = ~CLK;

        end

endmodule

```

FIGURE 15: RESULT STAGE 2 SELF-TEST ALU CODE

## RISING AN ERROR

As we can see below in the wave form, by introducing an error the result will be wrong, and the system will discover it and rise an error.

 


FIGURE 16: RESULT STAGE 2 ERROR WAVE

```

◦ # KERNEL: Error Occured at TIME = 900000
◦ # KERNEL: Error Occured at TIME = 1100000
◦ # KERNEL: Error Occured at TIME = 2500000
◦ # KERNEL: Error Occured at TIME = 2700000
◦ # KERNEL: Error Occured at TIME = 4100000

```

FIGURE 17: RESULT STAGE 2 ERROR OCCURED

## 4.CONCLUSION AND FUTURE WORKS

In conclusion we learned how to structurally make a 4-bit Arithmetic Unit that can implement deferent microoperation and how to check and verify if our work is done accurately.

The two stages presented that there is always more than a way to implement circuit that gave the same result, yet each implementation has its own advantages and disadvantages, in time or the number of needed gates needed, and some can be considered better than others judging based on results.

This project helped me develop new skills in Verilog hardware description language that make me implement very complex circuits than before, in addition to taking advantage of its capability to run in parallel to make things go faster.

# APPENDIX

## CODE

```
`timescale 1ns / 1ps

/*
*****
***** */

/*

        Nicola Abu Shaibeh 1190843
        4 bit Arithmetic Unit
        12/08/2022
        The task is to design an Arithmetic Unit

*/

/*
*****
***** */

module mux (out, a, b, c, d, s0, s1);
    output out;
    input a, b, c, d, s0, s1;
    wire sobar, s1bar, T1, T2, T3, T4;

    not #(3ns) (s0bar, s0), (s1bar, s1);
    and #(7ns) (T1, a, s0bar, s1bar), (T2, b, s0bar, s1), (T3, c, s0, s1bar), (T4, d, s0, s1);
    or #(7ns) (out, T1, T2, T3, T4);

endmodule

/*
*****
***** */
```

```
module full_adder(a,b,cin,s,cout); // Full adder module for ripple carry 4 bit adder
```

```
    input a,b,cin;
```

```
    output cout,s;
```

```
    wire [2:0]w;
```

```
    xor #(12ns) x1(w[0],a,b);
```

```
    xor #(12ns) x2(s,w[0],cin);
```

```
    and #(8ns) a1(w[1],w[0],cin);
```

```
    and #(8ns) a2(w[2],a,b);
```

```
    or #(8ns) o1(cout,w[1],w[2]);
```

```
endmodule
```

```
module ripple_carry_adder(a,b,s,cin,cout);
```

```
    input [3:0]a;
```

```
    input [3:0]b;
```

```
    input cin;
```

```
    output [3:0]s;
```

```
    output cout;
```

```
    wire [3:0]C;
```

```
    full_adder f1(a[0],b[0],cin,s[0],C[0]);
```

```
    full_adder f2(a[1],b[1],C[0],s[1],C[1]);
```

```
    full_adder f3(a[2],b[2],C[1],s[2],C[2]);
```

```
    full_adder f4(a[3],b[3],C[2],s[3],cout);
```

```
endmodule
```

```
/*
```

```
*****
```

```
***** */
```



```

module DFF (Q,D,CLK);
    output Q;
    input D,CLK;
    reg Q;
    always @(posedge CLK)
        Q = D;
endmodule

```

```

module registerIN(Q,D,CLK);
    parameter n = 15;
    input [n-1:0]D;
    input CLK;
    output [n-1:0]Q;

    genvar i;

    generate
        for (i=0;i<=n-1;i=i+1)
            begin:addbit
                DFF stage(Q[i],D[i],CLK);
            end
        endgenerate
endmodule

```

```

module registerOUT(Q,D,CLK);
    parameter n = 5;
    input [n-1:0]D;
    input CLK;
    output [n-1:0]Q;

```

```

        genvar i;

        generate
        for (i=0;i<=n-1;i=i+1)
            begin:addbit
                DFF stage(Q[i],D[i],CLK);
            end
        endgenerate
    endmodule

    /*
    ****
    **** */

    module ALU(a, b, d, s0, s1, cin, cout, CLK);
        input [3:0] a, b;
        input s0, s1, cin, CLK;
        output [3:0] d;
        output cout;
        wire [3:0] A, B, Bnot, D;
        wire S0, S1, CIN, COUT;
        wire [3:0] c;
        reg [3:0] bnot;
        assign bnot = ~b;
        assign zero = 1'b0;
        assign one = 1'b1;

        // 0-3a 4-7b, 8-11!b 12s0 13s1 14cin
        registerIN ri({A,B,Bnot,S0,S1,CIN},{a, b, bnot, s0, s1, cin},CLK);

        mux m0(c[0], B[0], Bnot[0], zero, one, S0, S1);
    
```

```

mux m1(c[1], B[1], Bnot[1], zero, one, S0, S1);
mux m2(c[2], B[2], Bnot[2], zero, one, S0, S1);
mux m3(c[3], B[3], Bnot[3], zero, one, S0, S1);
ripple_carry_adder fr(A[3:0],c[3:0],D[3:0],CIN,COUT);

registerOUT #(.n(18)) ro({cout, d},{COUT, D},CLK);

endmodule

module Stimulus() ;
    reg [3:0] a,b;
    reg s0,s1,cin, CLK;
    wire [3:0] d;
    wire cout;
    ALU my(.a(a),.b(b),.d(d),.s0(s0),.s1(s1),.cin(cin), .cout(cout), .CLK(CLK));

    initial
        begin
            CLK=0;
            repeat(2000)
                #100ns CLK = ~CLK;
            $finish;
        end

    initial
        begin
            a = 4'b1010;
            b = 4'b0101;

            {s0, s1, cin} = 3'b000;
        end
endmodule

```

```

        #100ns;
        repeat(7)
            #200ns {s0, s1, cin} = {s0, s1, cin} + 3'b001;

        $display("s0 = %b , s1 = %b , cin = %b \n",s0,s1,cin);
        $display("ANSWER = %b %b %b %b\n",d[3],d[2],d[1],d[0]);

    end
endmodule

/*
*****
***** */

module LookAhead(A,B,c_0,S,c_4);
    input [3:0]A,B;
    input c_0;
    output [3:0]S;
    output c_4;
    wire [3:0]P,G;
    wire [3:1]C;
    wire [3:0]w;
    wire [3:0]ig;

    //propagation and generator implementation
    xor #(11ns) x1(P[0],A[0],B[0]);
    xor #(11ns) x2(P[1],A[1],B[1]);
    xor #(11ns) x3(P[2],A[2],B[2]);
    xor #(11ns) x4(P[3],A[3],B[3]);

    and #(7ns) a1(G[0],A[0],B[0]);
    and #(7ns) a2(G[1],A[1],B[1]);
    and #(7ns) a3(G[2],A[2],B[2]);
    and #(7ns) a4(G[3],A[3],B[3]);

```

```

//fulladder to get sum with carry out ignorant
full_adder f1(A[0],B[0],c_0,S[0],ig[0]);
full_adder f2(A[1],B[1],C[1],S[1],ig[1]);
full_adder f3(A[2],B[2],C[2],S[2],ig[2]);
full_adder f4(A[3],B[3],C[3],S[3],ig[3]);

//carries implementation
and #(7ns) a5(w[0],P[0],c_0);
or #(7ns) o1(C[1],G[0],w[0]);

and #(7ns) a7(w[1],P[1],C[1]);
and #(7ns) a8(w[2],P[2],C[2]);
and #(7ns) a9(w[3],P[3],C[3]);

or #(7ns) o2(C[2],G[1],w[1]);
or #(7ns) o3(C[3],G[2],w[2]);
or #(7ns) o4(c_4,G[3],w[3]);

endmodule

```

```

module ALU_LA(a, b, d, s0, s1, cin, cout, CLK);
    input [3:0] a, b;
    input s0, s1, cin, CLK;
    output [3:0] d;
    output cout;
    wire [3:0] A, B, Bnot, D;
    wire S0, S1, CIN, COUT;
    wire [3:0] c;
    reg [3:0] bnot;
    assign bnot = ~b;
    assign zero = 1'b0;
    assign one = 1'b1;

```

```

// 0-3a 4-7b, 8-11!b 12s0 13s1 14cin
registerIN ri({A,B,Bnot,S0,S1,CIN},{a, b, bnot, s0, s1, cin},CLK);

mux m0(c[0], B[0], Bnot[0], zero, one, S0, S1);
mux m1(c[1], B[1], Bnot[1], zero, one, S0, S1);
mux m2(c[2], B[2], Bnot[2], zero, one, S0, S1);
mux m3(c[3], B[3], Bnot[3], zero, one, S0, S1);

LookAhead la(A[3:0],c[3:0],CIN,D[3:0],COUT);
registerOUT #(.n(18)) ro({cout, d},{COUT, D},CLK);

endmodule

module Stimulus_LA() ;
    reg [3:0] a,b;
    reg s0,s1,cin, CLK;
    wire [3:0] d;
    wire cout;
    ALULA myla(.a(a),.b(b),.d(d),.s0(s0),.s1(s1),.cin(cin), .cout(cout), .CLK(CLK));

    initial
        begin
            CLK=0;
            repeat(2000)
                #100ns CLK = ~CLK;
            $finish;
        end

    initial
        begin
            a = 4'b1010;
            b = 4'b0101;
        end
endmodule

```

```

        {s0, s1, cin} = 3'b000;
        #100ns;
        repeat(7)
            #200ns {s0, s1, cin} = {s0, s1, cin} + 3'b001;

        $display("s0 = %b , s1 = %b , cin = %b \n",s0,s1,cin);
        $display("ANSWER = %b %b %b %b\n",d[3],d[2],d[1],d[0]);

    end
endmodule

/*
*****
***** */

module TestGenerator(a, b, d, s0, s1, cin, cout, CLK);
    input CLK;
    output reg [3:0] a, b;
    output reg s0, s1, cin;
    output reg [3:0] d;
    output cout;
    assign bnot = ~b;
    always @(posedge CLK)

        begin
            case({s0,s1,cin})
                3'b000: d = a + b;
                3'b001: d = a + b + 1'b1;
                3'b010: d = a + bnot;
                3'b011: d = a + bnot + 1'b1;
            endcase
        end
endmodule

```

```

        3'b100: d = a;
        3'b101: d = a + 1'b1;
        3'b110: d = a - 1'b1;
        3'b111: d = a;
    endcase

    {s0, s1, cin} = {s0, s1, cin} + 3'b001;

end

initial
    begin
        a = 4'b0100;
        b = 4'b0010;
        {s0, s1, cin} = 3'b000;
    end

endmodule

module TestAnalyzer(CLK,genin,circin);
    input CLK;
    input [3:0]genin;
    input [3:0]circin;

    reg [8:0]check;

    always @(posedge CLK)
        begin
            if (check != circin)
                begin
                    $display("Error Occured at TIME = %t", $time);
                    //$finish;
                end
        end
endmodule

```



```

        end

        check = genin;
    end
endmodule

module SelfTestALU();
    reg CLK;
    reg [3:0] a,b;
    reg s0,s1,cin;
    wire [3:0]circuit_out,generator_out;
    reg cout, Cout;

    generator g(a, b, generator_out, s0, s1, cin, cout, CLK);

    ALU al(a, b, circuit_out, s0, s1, cin, Cout, CLK);

    analayzer z(CLK,generator_out,circuit_out);

    initial
        begin

            CLK = 0;
            repeat(200)
                #100ns CLK = ~CLK;
        end

endmodule

module SelfTestALU_LA();
    reg CLK;
    reg [3:0] a,b;

```

```

reg s0,s1,cin;
wire [3:0]circuit_out,generator_out;
reg cout, Cout;

generator g(a, b, generator_out, s0, s1, cin, cout, CLK);

ALU_LA la(a, b, circuit_out, s0, s1, cin, Cout, CLK);

analyzzer z(CLK,generator_out,circuit_out);

initial
    begin

        CLK = 0;
        repeat(200)
            #100ns CLK = ~CLK;

    end

endmodule

/*
*****
***** */

```